



台灣新竹·交通大學·電機與控制工程研究所·808實驗室
電力電子系統晶片、數位電源、DSP控制、馬達與伺服控制
Lab-808: Power Electronic Systems & Chips Lab., NCTU, Taiwan
<http://pemclab.cn.nctu.edu.tw/>

808-PowerLab NCTU HSINCHU TAIWAN

State-Space Averaging Technique

鄒應嶼 教授

國立交通大學 電機與控制工程研究所


2009年5月15日



Lab808: 電力電子系統與晶片實驗室
Power Electronic Systems & Chips, NCTU, TAIWAN
台灣新竹·交通大學·電機與控制工程研究所

1/45


State-Space Averaging Techniques






- State Space Averaging Modeling
- Static Analysis
- Small-Signal Model at CCM
- Small-Signal Model at DCM
- Frequency Response Analysis

808-PowerLab NCTU HSINCHU TAIWAN

2/45

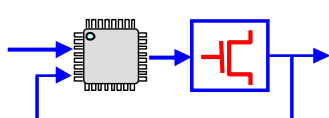

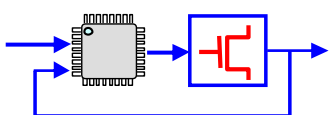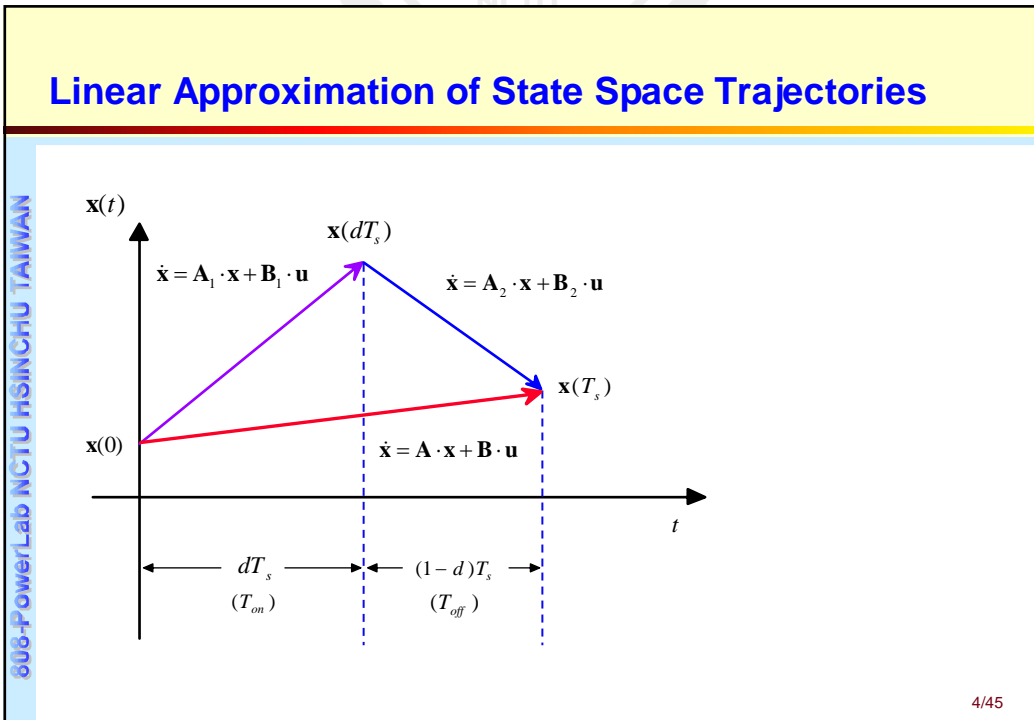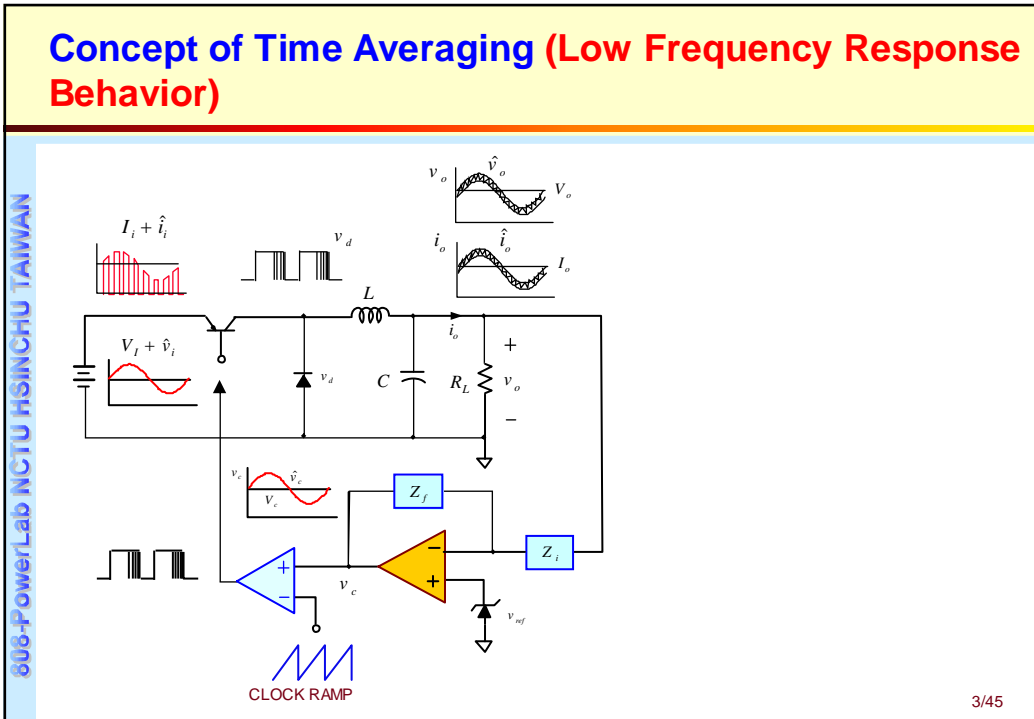

808-PowerLab NCTU HSINCHU TAIWAN

State-Space Averaging Method (CCM)

During T_{ON}

$$\begin{cases} \dot{\mathbf{x}} = \mathbf{A}_1\mathbf{x} + \mathbf{B}_1\mathbf{u} \\ \mathbf{y} = \mathbf{C}_1\mathbf{x} + \mathbf{E}_1\mathbf{u} \end{cases}$$

During T_{OFF}

$$\begin{cases} \dot{\mathbf{x}} = \mathbf{A}_2\mathbf{x} + \mathbf{B}_2\mathbf{u} \\ \mathbf{y} = \mathbf{C}_2\mathbf{x} + \mathbf{E}_2\mathbf{u} \end{cases}$$

When the circuit time constant is far greater than the switching period, the above equations can be averaged as:

Switch-ON Period

$$\begin{cases} \dot{\mathbf{x}} = \mathbf{A}_1\mathbf{x} + \mathbf{B}_1\mathbf{u} \\ \mathbf{y} = \mathbf{C}_1\mathbf{x} + \mathbf{E}_1\mathbf{u} \end{cases}$$

$\times d_1$


Switch-OFF Period

$$\begin{cases} \dot{\mathbf{x}} = \mathbf{A}_2\mathbf{x} + \mathbf{B}_2\mathbf{u} \\ \mathbf{y} = \mathbf{C}_2\mathbf{x} + \mathbf{E}_2\mathbf{u} \end{cases}$$

$\times d_2$

averaging by using state duty ratio weighting

5/45

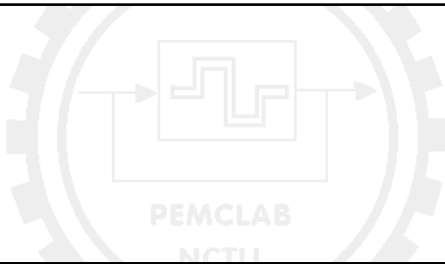

808-PowerLab NCTU HSINCHU TAIWAN

State-Space Averaging Method


$$\dot{\mathbf{x}} = (\mathbf{A}_1d_1 + \mathbf{A}_2d_2)\mathbf{x} + (\mathbf{B}_1d_1 + \mathbf{B}_2d_2)\mathbf{u}$$

$$\mathbf{y} = (\mathbf{C}_1d_1 + \mathbf{C}_2d_2)\mathbf{x} + (\mathbf{E}_1d_1 + \mathbf{E}_2d_2)\mathbf{u}$$

$\mathbf{x} = \mathbf{A}\mathbf{x} + \mathbf{B}\mathbf{u}$
 $\mathbf{y} = \mathbf{C}\mathbf{x} + \mathbf{D}\mathbf{u}$
 where

$\mathbf{A} = \mathbf{A}_1d_1 + \mathbf{A}_2d_2$
 $\mathbf{B} = \mathbf{B}_1d_1 + \mathbf{B}_2d_2$
 $\mathbf{C} = \mathbf{C}_1d_1 + \mathbf{C}_2d_2$
 $\mathbf{E} = \mathbf{E}_1d_1 + \mathbf{E}_2d_2$

6/45

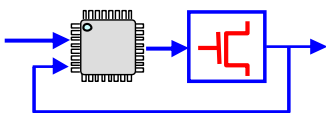

State Averaging by Active Duty Ratios

During T_{ON} $\begin{cases} \dot{\mathbf{x}} = \mathbf{A}_1\mathbf{x} + \mathbf{B}_1\mathbf{u} \\ \mathbf{y} = \mathbf{C}_1\mathbf{x} + \mathbf{E}_1\mathbf{u} \end{cases}$

During T_{OFF} $\begin{cases} \dot{\mathbf{x}} = \mathbf{A}_2\mathbf{x} + \mathbf{B}_2\mathbf{u} \\ \mathbf{y} = \mathbf{C}_2\mathbf{x} + \mathbf{E}_2\mathbf{u} \end{cases}$

When the circuit time constant is far greater than the switching period, the above equations can be averaged as:

Switch-ON Period

$$\begin{cases} \dot{\mathbf{x}} = \mathbf{A}_1\mathbf{x} + \mathbf{B}_1\mathbf{u} \\ \mathbf{y} = \mathbf{C}_1\mathbf{x} + \mathbf{E}_1\mathbf{u} \end{cases}$$

Switch-OFF Period

$$\begin{cases} \dot{\mathbf{x}} = \mathbf{A}_2\mathbf{x} + \mathbf{B}_2\mathbf{u} \\ \mathbf{y} = \mathbf{C}_2\mathbf{x} + \mathbf{E}_2\mathbf{u} \end{cases}$$

state averaging by using duty ratio weighting

↓

$$\begin{aligned} \dot{\mathbf{x}} &= (\mathbf{A}_1d_1 + \mathbf{A}_2d_2)\mathbf{x} + (\mathbf{B}_1d_1 + \mathbf{B}_2d_2)\mathbf{u} \\ \mathbf{y} &= (\mathbf{C}_1d_1 + \mathbf{C}_2d_2)\mathbf{x} + (\mathbf{E}_1d_1 + \mathbf{E}_2d_2)\mathbf{u} \end{aligned}$$

$\mathbf{x} = \mathbf{A}\mathbf{x} + \mathbf{B}\mathbf{u}$
 $\mathbf{y} = \mathbf{C}\mathbf{x} + \mathbf{D}\mathbf{u}$
 where

$$\begin{aligned} \mathbf{A} &= \mathbf{A}_1d_1 + \mathbf{A}_2d_2 \\ \mathbf{B} &= \mathbf{B}_1d_1 + \mathbf{B}_2d_2 \\ \mathbf{C} &= \mathbf{C}_1d_1 + \mathbf{C}_2d_2 \\ \mathbf{E} &= \mathbf{E}_1d_1 + \mathbf{E}_2d_2 \end{aligned}$$

7/45

Small-Signal Perturbation at a DC Operating Point

Substitute $\mathbf{x} = \mathbf{X} + \hat{\mathbf{x}}$; $\mathbf{y} = \mathbf{Y} + \hat{\mathbf{y}}$; $\mathbf{u} = \mathbf{U} + \hat{\mathbf{u}}$;
 $d_1 = D_1 + \hat{d}$; $d_2 = D_2 - \hat{d}$

$$\frac{d}{dt}(\mathbf{X} + \hat{\mathbf{x}}) = [\mathbf{A}_1(D_1 + \hat{d}) + \mathbf{A}_2(D_2 - \hat{d})](\mathbf{X} + \hat{\mathbf{x}}) + [\mathbf{B}_1(D_1 + \hat{d}) + \mathbf{B}_2(D_2 - \hat{d})](\mathbf{U} + \hat{\mathbf{u}})$$

$$\underbrace{\frac{d}{dt}\mathbf{X}}_{\text{dc terms}=0} + \frac{d}{dt}\hat{\mathbf{x}} = \underbrace{(\mathbf{A}_1D_1 + \mathbf{A}_2D_2)\mathbf{X} + (\mathbf{B}_1D_1 + \mathbf{B}_2D_2)\mathbf{U}}_{\text{dc terms}=0} +$$


$$(\mathbf{A}_1D_1 + \mathbf{A}_2D_2)\hat{\mathbf{x}} + (\mathbf{B}_1D_1 + \mathbf{B}_2D_2)\hat{\mathbf{u}} +$$

$$[(\mathbf{A}_1 - \mathbf{A}_2)\mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2)\mathbf{U}]\hat{d} +$$

$$\underbrace{(\mathbf{A}_1 - \mathbf{A}_2)\hat{d}\hat{\mathbf{x}} + (\mathbf{B}_1 - \mathbf{B}_2)\hat{d}\hat{\mathbf{u}}}_{\text{ignore nonlinear term}}$$

Note:
 The nonlinear dynamic system is linearized around a selected operating point!

8/45

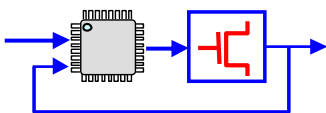

DC Model and AC Model

DC Model

$$\mathbf{X} = -\mathbf{A}^{-1}\mathbf{B}\mathbf{U}$$

$$\mathbf{Y} = (-\mathbf{C}\mathbf{A}^{-1}\mathbf{B} + \mathbf{E})\mathbf{U}$$

AC Model

$$\frac{d}{dt}\hat{\mathbf{x}} = \mathbf{A}\hat{\mathbf{x}} + \mathbf{B}\hat{\mathbf{u}} + \mathbf{F}\hat{d}$$

$$\hat{\mathbf{y}} = \mathbf{C}\hat{\mathbf{x}} + \mathbf{E}\hat{\mathbf{u}} + \mathbf{G}\hat{d}$$

where

$$\mathbf{A} = \mathbf{A}_1D_1 + \mathbf{A}_2D_2$$

$$\mathbf{B} = \mathbf{B}_1D_1 + \mathbf{B}_2D_2$$


$$\mathbf{C} = \mathbf{C}_1D_1 + \mathbf{C}_2D_2$$

$$\mathbf{E} = \mathbf{E}_1D_1 + \mathbf{E}_2D_2$$

$$\mathbf{F} = (\mathbf{A}_1 - \mathbf{A}_2)\mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2)\mathbf{U}$$

$$\mathbf{G} = (\mathbf{C}_1 - \mathbf{C}_2)\mathbf{X} + (\mathbf{E}_1 - \mathbf{E}_2)\mathbf{U}$$

9/45

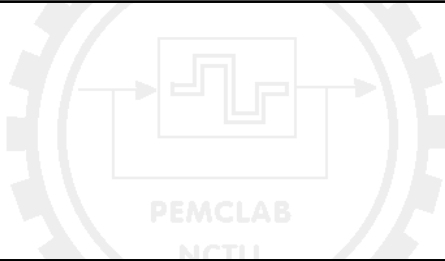

Transfer Function Matrix

$$\mathbf{x}(s) = (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B}\mathbf{u}(s) + (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{F}d(s)$$

$$= \mathbf{H}_u(s)\mathbf{u}(s) + \mathbf{H}_d(s)d(s)$$

$$\mathbf{H}_u(s) = (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B}$$

$$\mathbf{H}_d(s) = (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{F}$$

$$\mathbf{y}(s) = [\mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B} + \mathbf{E}]\mathbf{u}(s) + [\mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{F} + \mathbf{G}]d(s)$$


$$= \mathbf{G}_u(s)\mathbf{u}(s) + \mathbf{G}_d(s)d(s)$$

$$\mathbf{G}_u(s) = \mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B} + \mathbf{E}$$

$$\mathbf{G}_d(s) = \mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{F} + \mathbf{G}$$

$$\begin{bmatrix} v_o(s) \\ i_i(s) \end{bmatrix} = \begin{bmatrix} G_{u11}(s) & G_{u12}(s) \\ G_{u21}(s) & G_{u22}(s) \end{bmatrix} \begin{bmatrix} v_i(s) \\ i_d(s) \end{bmatrix} + \begin{bmatrix} G_{d1}(s) \\ G_{d2}(s) \end{bmatrix} d(s)$$

10/45

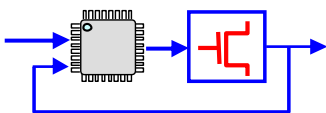

Open Loop Transfer Functions


- control-to-output (open-loop transfer function):

$$\frac{v_o(s)}{d(s)} = G_{d1}(s) = \mathbf{G}_d(s) \Big|_1 = \left[\mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1} \mathbf{F} + \mathbf{G} \right]_1$$
- line-to-output (audio susceptibility):

$$\frac{v_o(s)}{v_i(s)} = G_{u1}(s) = \mathbf{G}_u(s) \Big|_{11} = \left[\mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1} \mathbf{B} + \mathbf{E} \right]_{11}$$
- output impedance:

$$\frac{v_o(s)}{i_d(s)} = G_{u2}(s) = \mathbf{G}_u(s) \Big|_{12} = \left[\mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1} \mathbf{B} + \mathbf{E} \right]_{12}$$

11/45

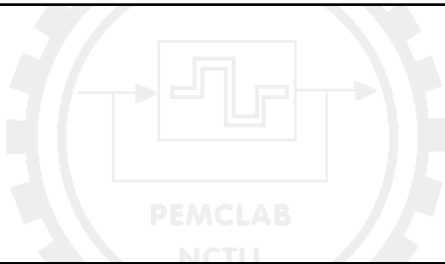


Example: Buck Converter

Step 1. Draw the linear equivalent circuit for each switching state of the converter.

Q closed, D open

D closed, Q open

12/45

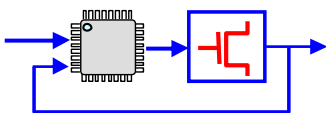

Select State Variables

Select the inductor current i_L and capacitor voltage v_C state variables.

$$\mathbf{x} = \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} = \begin{bmatrix} i_L \\ v_C \end{bmatrix}$$

Select the input dc voltage and output disturbance current as input variables.

$$\mathbf{u} = \begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \begin{bmatrix} v_i \\ i_d \end{bmatrix}$$

Select the output voltage and input current as output variables.

$$\mathbf{y} = \begin{bmatrix} y_1 \\ y_2 \end{bmatrix} = \begin{bmatrix} v_o \\ i_i \end{bmatrix}$$

13/45

Derive Circuit Equations: State Equations

Step 2. Write the circuit equations for each equivalent circuit in a state-variable format.

Q-ON and D-OFF State:


- ① $v_i = L \frac{di_L}{dt} + i_L r_L + r_c C \frac{dv_C}{dt} + v_C$
- ② $r_c C \frac{dv_C}{dt} + v_C = (i_L - i_c - i_d)R$
 $= (i_L - C \frac{dv_C}{dt} + i_d)R$
 $= i_L R - RC \frac{dv_C}{dt} + i_d R$

$$(R + r_c)C \frac{dv_C}{dt} = i_L R - v_C - i_d R$$

↓

$$\frac{dv_C}{dt} = \frac{R}{(R+r_c)C} i_L - \frac{1}{(R+r_c)C} v_C - \frac{R}{(R+r_c)C} i_d$$

14/45

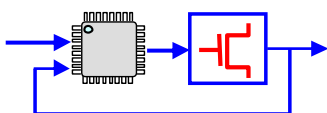

808-PowerLab NCTU HSINCHU TAIWAN

State-Space Average Modeling: State Equations

Replace $C \frac{dv_c}{dt}$ in ❶ with $\frac{R}{(R+r_c)}i_L - \frac{1}{(R+r_c)}v_c - \frac{R}{(R+r_c)}i_d$

We can obtain:

$$v_i = L \frac{di_L}{dt} + i_L r_L + r_c \left(\frac{R}{(R+r_c)}i_L - \frac{1}{(R+r_c)}v_c - \frac{R}{(R+r_c)}i_d \right) + v_c$$

$$L \frac{di_L}{dt} = v_i - i_L r_L - \frac{R r_c}{(R+r_c)}i_L + \frac{r_c}{(R+r_c)}v_c - \frac{R r_c}{(R+r_c)}i_d - v_c$$

$$= \left(-\frac{R r_c}{R+r_c} + r_L \right) i_L - \left(\frac{R}{R+r_c} \right) v_c + v_i - \frac{R r_c}{R+r_c} i_d$$

↓

$$\frac{di_L}{dt} = -\frac{1}{L} \left(\frac{R r_c}{R+r_c} + r_L \right) i_L - \frac{1}{L} \left(\frac{R}{R+r_c} \right) v_c + \frac{1}{L} v_i - \frac{1}{L} \left(\frac{R r_c}{R+r_c} \right) i_d$$

15/45

808-PowerLab NCTU HSINCHU TAIWAN

State-Space Average Modeling: State Equations

❸ $i_i = i_L$

❹ $v_o = (i_L - i_c - i_d)R$
 $= i_L R - i_c R - i_d R$

$$= i_L R - R C \left(\frac{R}{(R+r_c)}i_L - \frac{1}{(R+r_c)}v_c - \frac{R}{(R+r_c)}i_d \right) - i_d R$$

$$v_o = \frac{R r_c}{(R+r_c)}i_L + \frac{R}{(R+r_c)}v_c - \frac{R r_c}{(R+r_c)}i_d$$


$$= \frac{R r_c}{(R+r_c)}i_L + \frac{R}{(R+r_c)}v_c - \frac{R r_c}{(R+r_c)}i_d$$

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_c \end{bmatrix} = \begin{bmatrix} -\frac{1}{L} \left(\frac{R r_c}{R+r_c} + r_L \right) & -\frac{1}{L} \left(\frac{R}{R+r_c} \right) \\ \frac{1}{C} \left(\frac{R}{R+r_c} \right) & -\frac{1}{C} \left(\frac{1}{R+r_c} \right) \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} \frac{1}{L} & -\frac{1}{L} \left(\frac{R r_c}{R+r_c} \right) \\ 0 & -\frac{1}{C} \left(\frac{R}{R+r_c} \right) \end{bmatrix} \begin{bmatrix} v_i \\ i_d \end{bmatrix}$$

$$\begin{bmatrix} v_o \\ \dot{i}_i \end{bmatrix} = \begin{bmatrix} \frac{R r_c}{R+r_c} & \frac{R}{R+r_c} \\ 1 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} 0 & -\frac{R r_c}{R+r_c} \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_i \\ i_d \end{bmatrix}$$

Q-OFF and D-ON State Equation

16/45

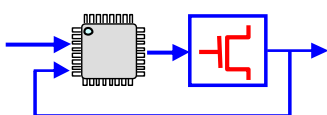

State-Space Average Modeling: State Equations

Q-OFF and D-ON State:

- 1 $0 = L \frac{di_L}{dt} + i_L r_L + r_c C \frac{dv_c}{dt} + v_c$
- 2 $r_c C \frac{dv_c}{dt} + v_c = (i_L - i_c - i_d) R$
 $= (i_L - C \frac{dv_c}{dt} - i_d) R$
 $= i_L R - RC \frac{dv_c}{dt} - i_d R$

$$(R+r_c)C \frac{dv_c}{dt} = i_L R - v_c - i_d R$$

↓

$$\frac{dv_c}{dt} = -\frac{R}{(R+r_c)C} i_L - \frac{1}{(R+r_c)C} v_c - \frac{R}{(R+r_c)C} i_d$$

17/45

State-Space Average Modeling: State Equations

Q-OFF and D-ON State:

- 1 $0 = L \frac{di_L}{dt} + i_L r_L + r_c C \frac{dv_c}{dt} + v_c$
- 2 $r_c C \frac{dv_c}{dt} + v_c = (i_L - i_c - i_d) R$
 $= (i_L - C \frac{dv_c}{dt} - i_d) R$
 $= i_L R - RC \frac{dv_c}{dt} - i_d R$

$$(R+r_c)C \frac{dv_c}{dt} = i_L R - v_c - i_d R$$

↓

$$\frac{dv_c}{dt} = -\frac{R}{(R+r_c)C} i_L - \frac{1}{(R+r_c)C} v_c - \frac{R}{(R+r_c)C} i_d$$

Replace $C \frac{dv_c}{dt}$ in **1** with $\frac{R}{(R+r_c)} i_L - \frac{1}{(R+r_c)} v_c - \frac{R}{(R+r_c)} i_d$

We can obtain: $0 = L \frac{di_L}{dt} + i_L r_L + r_c \left(\frac{R}{(R+r_c)} i_L - \frac{1}{(R+r_c)} v_c - \frac{R}{(R+r_c)} i_d \right) + v_c$


↓

$$L \frac{di_L}{dt} = -i_L r_L - \frac{R r_c}{(R+r_c)} i_L + \frac{r_c}{(R+r_c)} v_c - \frac{R r_c}{(R+r_c)} i_d - v_c$$

⇒

$$\frac{di_L}{dt} = -\frac{1}{L} \left(\frac{R r_c}{R+r_c} + r_L \right) i_L - \frac{1}{L} \left(\frac{R}{R+r_c} \right) v_c - \frac{1}{L} \left(\frac{R r_c}{R+r_c} \right) i_d$$

18/45

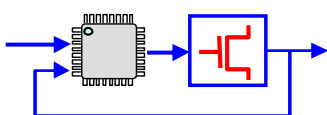

State-Space Average Modeling: State Equations

③ $i_i = 0$

④ $v_o = (i_L - i_c - i_d)R$
 $= i_L R - i_c R - i_d R$
 $= i_L R - RC \left(\frac{R}{(R+r_c)C} i_L - \frac{1}{(R+r_c)C} v_c - \frac{R}{(R+r_c)C} i_d \right) - i_d R$
 $= \frac{Rr_c}{(R+r_c)} i_L + \frac{R}{(R+r_c)} v_c - \frac{Rr_c}{(R+r_c)} i_d$


$$v_o = \frac{Rr_c}{(R+r_c)} i_L + \frac{R}{(R+r_c)} v_c - \frac{Rr_c}{(R+r_c)} i_d$$

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_c \end{bmatrix} = \begin{bmatrix} -\frac{1}{L} \left(\frac{Rr_c}{R+r_c} + r_L \right) & -\frac{1}{L} \left(\frac{R}{R+r_c} \right) \\ \frac{1}{C} \left(\frac{R}{R+r_c} \right) & -\frac{1}{C} \left(\frac{1}{R+r_c} \right) \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} 0 & -\frac{1}{L} \left(\frac{Rr_c}{R+r_c} \right) \\ 0 & -\frac{1}{C} \left(\frac{R}{R+r_c} \right) \end{bmatrix} \begin{bmatrix} v_i \\ i_d \end{bmatrix}$$

$$\begin{bmatrix} v_o \\ i_i \end{bmatrix} = \begin{bmatrix} \frac{Rr_c}{R+r_c} & \frac{R}{R+r_c} \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} 0 & -\frac{Rr_c}{R+r_c} \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_i \\ i_d \end{bmatrix}$$

Q-ON and D-OFF State Equation

19/45

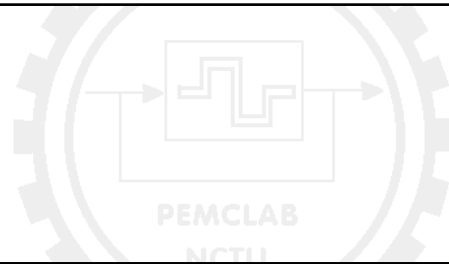

State-Space Average Modeling: State Equations

Q Conducted:

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_c \end{bmatrix} = \begin{bmatrix} -\frac{1}{L} \left(\frac{Rr_c}{R+r_c} + r_L \right) & -\frac{1}{L} \left(\frac{R}{R+r_c} \right) \\ \frac{1}{C} \left(\frac{R}{R+r_c} \right) & -\frac{1}{C} \left(\frac{1}{R+r_c} \right) \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} \frac{1}{L} & -\frac{1}{L} \left(\frac{Rr_c}{R+r_c} \right) \\ 0 & -\frac{1}{C} \left(\frac{R}{R+r_c} \right) \end{bmatrix} \begin{bmatrix} v_i \\ i_d \end{bmatrix}$$


$$\begin{bmatrix} v_o \\ i_i \end{bmatrix} = \begin{bmatrix} \frac{Rr_c}{R+r_c} & \frac{R}{R+r_c} \\ 1 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} 0 & -\frac{Rr_c}{R+r_c} \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_i \\ i_d \end{bmatrix}$$

D Conducted:

$$\begin{bmatrix} \dot{i}_L \\ \dot{v}_c \end{bmatrix} = \begin{bmatrix} -\frac{1}{L} \left(\frac{Rr_c}{R+r_c} + r_L \right) & -\frac{1}{L} \left(\frac{R}{R+r_c} \right) \\ \frac{1}{C} \left(\frac{R}{R+r_c} \right) & -\frac{1}{C} \left(\frac{1}{R+r_c} \right) \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} 0 & -\frac{1}{L} \left(\frac{Rr_c}{R+r_c} \right) \\ 0 & -\frac{1}{C} \left(\frac{R}{R+r_c} \right) \end{bmatrix} \begin{bmatrix} v_i \\ i_d \end{bmatrix}$$

$$\begin{bmatrix} v_o \\ i_i \end{bmatrix} = \begin{bmatrix} \frac{Rr_c}{R+r_c} & \frac{R}{R+r_c} \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v_c \end{bmatrix} + \begin{bmatrix} 0 & -\frac{Rr_c}{R+r_c} \\ 0 & 0 \end{bmatrix} \begin{bmatrix} v_i \\ i_d \end{bmatrix}$$

20/45

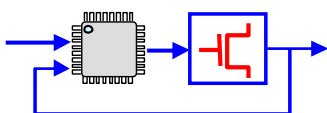

State-Space Average Modeling: State Equations

Q Conducted:

$$\mathbf{A}_1 = \begin{bmatrix} -\frac{1}{L} \left(\frac{Rr_c}{R+r_c} + r_L \right) & -\frac{1}{L} \left(\frac{R}{R+r_c} \right) \\ \frac{1}{C} \left(\frac{R}{R+r_c} \right) & -\frac{1}{C} \left(\frac{1}{R+r_c} \right) \end{bmatrix}, \quad \mathbf{B}_1 = \begin{bmatrix} \frac{1}{L} & -\frac{1}{L} \left(\frac{Rr_c}{R+r_c} \right) \\ 0 & -\frac{1}{C} \left(\frac{R}{R+r_c} \right) \end{bmatrix}$$

$$\mathbf{C}_1 = \begin{bmatrix} \frac{Rr_c}{R+r_c} & \frac{R}{R+r_c} \\ 1 & 0 \end{bmatrix}, \quad \mathbf{E}_1 = \begin{bmatrix} 0 & -\frac{Rr_c}{R+r_c} \\ 0 & 0 \end{bmatrix}$$

D Conducted:

$$\mathbf{A}_2 = \begin{bmatrix} -\frac{1}{L} \left(\frac{Rr_c}{R+r_c} + r_L \right) & -\frac{1}{L} \left(\frac{R}{R+r_c} \right) \\ \frac{1}{C} \left(\frac{R}{R+r_c} \right) & -\frac{1}{C} \left(\frac{1}{R+r_c} \right) \end{bmatrix}, \quad \mathbf{B}_2 = \begin{bmatrix} 0 & -\frac{1}{L} \left(\frac{Rr_c}{R+r_c} \right) \\ 0 & -\frac{1}{C} \left(\frac{R}{R+r_c} \right) \end{bmatrix}$$

$$\mathbf{C}_2 = \begin{bmatrix} \frac{Rr_c}{R+r_c} & \frac{R}{R+r_c} \\ 0 & 0 \end{bmatrix}, \quad \mathbf{E}_2 = \begin{bmatrix} 0 & -\frac{Rr_c}{R+r_c} \\ 0 & 0 \end{bmatrix}$$

21/45

State-Space Average Modeling: Averaging

Step 3. Average each state by using duty ratio as a weighting factor and then combine the two sets of equations into a single set.

$$\begin{aligned} Q: \dot{\mathbf{x}} &= \mathbf{A}_1 \mathbf{x} + \mathbf{B}_1 \mathbf{u} \\ \mathbf{y} &= \mathbf{C}_1 \mathbf{x} + \mathbf{E}_1 \mathbf{u} \end{aligned}$$

 $\times d_1$

+

$$\begin{aligned} D: \dot{\mathbf{x}} &= \mathbf{A}_2 \mathbf{x} + \mathbf{B}_2 \mathbf{u} \\ \mathbf{y} &= \mathbf{C}_2 \mathbf{x} + \mathbf{E}_2 \mathbf{u} \end{aligned}$$

 $\times d_2$

averaging by using state duty ratio weighting


$$\begin{aligned} \dot{\mathbf{x}} &= (\mathbf{A}_1 d_1 + \mathbf{A}_2 d_2) \mathbf{x} + (\mathbf{B}_1 d_1 + \mathbf{B}_2 d_2) \mathbf{u} \\ \mathbf{y} &= (\mathbf{C}_1 d_1 + \mathbf{C}_2 d_2) \mathbf{x} + (\mathbf{E}_1 d_1 + \mathbf{E}_2 d_2) \mathbf{u} \end{aligned}$$

$$\begin{aligned} \dot{\mathbf{x}} &= \mathbf{A} \mathbf{x} + \mathbf{B} \mathbf{u} \\ \mathbf{y} &= \mathbf{C} \mathbf{x} + \mathbf{E} \mathbf{u} \end{aligned}$$

where

$$\begin{aligned} \mathbf{A} &= \mathbf{A}_1 d_1 + \mathbf{A}_2 d_2 \\ \mathbf{B} &= \mathbf{B}_1 d_1 + \mathbf{B}_2 d_2 \\ \mathbf{C} &= \mathbf{C}_1 d_1 + \mathbf{C}_2 d_2 \\ \mathbf{E} &= \mathbf{E}_1 d_1 + \mathbf{E}_2 d_2 \end{aligned}$$

22/45

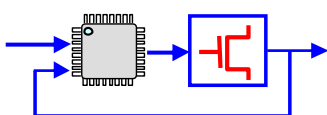

808-PowerLab NCTU HSINCHU TAIWAN

State-Space Average Modeling: Perturbation

Step 4. Perturb the averaged equation set to produce DC and small signal terms and eliminate nonlinear product terms.

Substitute $\mathbf{x} = \mathbf{X} + \hat{\mathbf{x}}$; $\mathbf{y} = \mathbf{Y} + \hat{\mathbf{y}}$; $\mathbf{u} = \mathbf{U} + \hat{\mathbf{u}}$;
 $d_1 = D_1 + \hat{d}$; $d_2 = D_2 - \hat{d}$

into the averaged equations (in Steps 3)

$$\dot{\mathbf{x}} = (\mathbf{A}_1 d_1 + \mathbf{A}_2 d_2) \mathbf{x} + (\mathbf{B}_1 d_1 + \mathbf{B}_2 d_2) \mathbf{u}$$

$$\mathbf{y} = (\mathbf{C}_1 d_1 + \mathbf{C}_2 d_2) \mathbf{x} + (\mathbf{E}_1 d_1 + \mathbf{E}_2 d_2) \mathbf{u}$$

$$\frac{d}{dt}(\mathbf{X} + \hat{\mathbf{x}}) = (\mathbf{A}_1(D_1 + \hat{d}) + \mathbf{A}_2(D_2 - \hat{d}))(\mathbf{X} + \hat{\mathbf{x}}) +$$

$$(\mathbf{B}_1(D_1 + \hat{d}) + \mathbf{B}_2(D_2 - \hat{d}))(\mathbf{U} + \hat{\mathbf{u}})$$


$$= \mathbf{A}_1 D_1 \mathbf{X} + \mathbf{A}_1 \hat{d} \mathbf{X} + \mathbf{A}_1 D_1 \hat{\mathbf{x}} + \mathbf{A}_1 \hat{d} \hat{\mathbf{x}} +$$

$$\mathbf{A}_2 D_2 \mathbf{X} - \mathbf{A}_2 \hat{d} \mathbf{X} + \mathbf{A}_2 D_2 \hat{\mathbf{x}} - \mathbf{A}_2 \hat{d} \hat{\mathbf{x}} +$$

$$\mathbf{B}_1 D_1 \mathbf{U} + \mathbf{B}_1 \hat{d} \mathbf{U} + \mathbf{B}_1 D_1 \hat{\mathbf{u}} + \mathbf{B}_1 \hat{d} \hat{\mathbf{u}} +$$

$$\mathbf{B}_2 D_2 \mathbf{U} - \mathbf{B}_2 \hat{d} \mathbf{U} + \mathbf{B}_2 D_2 \hat{\mathbf{u}} - \mathbf{B}_2 \hat{d} \hat{\mathbf{u}}$$

23/45

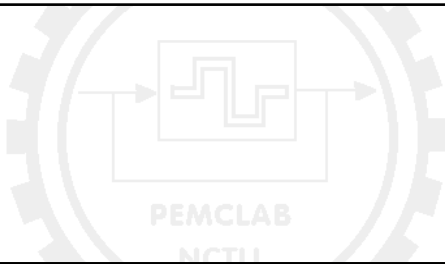

808-PowerLab NCTU HSINCHU TAIWAN

State-Space Average Modeling: Perturbation

Perturbation of the State Equations

$$\frac{d}{dt}(\mathbf{X} + \hat{\mathbf{x}}) = (\mathbf{A}_1 D_1 + \mathbf{A}_2 D_2) \mathbf{X} + (\mathbf{B}_1 D_1 + \mathbf{B}_2 D_2) \mathbf{U} +$$

$$(\mathbf{A}_1 D_1 + \mathbf{A}_2 D_2) \hat{\mathbf{x}} + (\mathbf{B}_1 D_1 + \mathbf{B}_2 D_2) \hat{\mathbf{u}} +$$

$$[(\mathbf{A}_1 - \mathbf{A}_2) \mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2) \mathbf{U}] \hat{d} +$$

$$(\mathbf{A}_1 - \mathbf{A}_2) \hat{d} \hat{\mathbf{x}} + (\mathbf{B}_1 - \mathbf{B}_2) \hat{d} \hat{\mathbf{u}}$$

$$\mathbf{Y} + \hat{\mathbf{y}} = (\mathbf{C}_1(D_1 + \hat{d}) + \mathbf{C}_2(D_2 - \hat{d}))(\mathbf{X} + \hat{\mathbf{x}}) +$$


$$(\mathbf{E}_1(D_1 + \hat{d}) + \mathbf{E}_2(D_2 - \hat{d}))(\mathbf{U} + \hat{\mathbf{u}})$$

$$= (\mathbf{C}_1 D_1 + \mathbf{C}_2 D_2) \mathbf{X} + (\mathbf{E}_1 D_1 + \mathbf{E}_2 D_2) \mathbf{U} +$$

$$(\mathbf{C}_1 D_1 + \mathbf{C}_2 D_2) \hat{\mathbf{x}} + [(\mathbf{C}_1 - \mathbf{C}_2) \mathbf{X} + (\mathbf{E}_1 - \mathbf{E}_2) \mathbf{U}] \hat{d} +$$

$$(\mathbf{E}_1 D_1 + \mathbf{E}_2 D_2) \hat{\mathbf{u}} + (\mathbf{C}_1 - \mathbf{C}_2) \hat{d} \hat{\mathbf{x}} + (\mathbf{E}_1 - \mathbf{E}_2) \hat{d} \hat{\mathbf{u}}$$

24/45

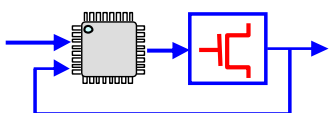

State-Space Average Modeling: DC Analysis

DC Analysis:

Set all variational terms to zero, we can obtain

$$0 = (\mathbf{A}_1 D_1 + \mathbf{A}_2 D_2) \mathbf{X} + (\mathbf{B}_1 D_1 + \mathbf{B}_2 D_2) \mathbf{U}$$

$$= \mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U}$$

$$\mathbf{Y} = (\mathbf{C}_1 D_1 + \mathbf{C}_2 D_2) \mathbf{X} + (\mathbf{E}_1 D_1 + \mathbf{E}_2 D_2) \mathbf{U}$$

$$= \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U}$$

Therefore

$$\mathbf{X} = -\mathbf{A}^{-1} \mathbf{B} \mathbf{U}$$

$$\mathbf{Y} = (-\mathbf{C} \mathbf{A}^{-1} \mathbf{B} + \mathbf{E}) \mathbf{U}$$

25/45

State-Space Average Modeling: DC Model

Eliminate the DC term $\frac{d}{dt} \mathbf{X} = 0 \rightarrow \mathbf{A} \mathbf{X} + \mathbf{B} \mathbf{U} = 0$ and $\mathbf{Y} = \mathbf{C} \mathbf{X} + \mathbf{E} \mathbf{U}$


We obtain the dc model equation:

$$D.C. \begin{cases} 0 = [-r_L + (R // r_C)] I_L - \left(\frac{R}{R + r_C} \right) V_C + V_i D \\ 0 = \left(\frac{R}{R + r_C} \right) I_L - \left(\frac{1}{R + r_C} \right) V_C \\ V_o = (R // r_C) I_L - \left(\frac{R}{R + r_C} \right) V_C \\ I_s = D I_L \end{cases}$$

Comments:

- DC model gives DC information (steady-state behavior).
- DC model can be used for loss estimation.

26/45

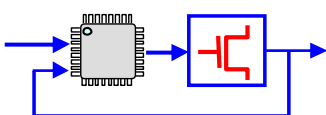

State-Space Average Modeling: AC Model

Neglect the nonlinear product term $\hat{d} \cdot \hat{x}$ and $\hat{d} \cdot \hat{u}$

We obtain the ac model (small-signal) equation:

$$\frac{d}{dt}\hat{x} = \mathbf{A}\hat{x} + \mathbf{B}\hat{u} + \mathbf{F}\hat{d}$$

$$\hat{y} = \mathbf{C}\hat{x} + \mathbf{E}\hat{u} + \mathbf{G}\hat{d}$$

where

$$\mathbf{A} = \mathbf{A}_1 D_1 + \mathbf{A}_2 D_2$$

$$\mathbf{B} = \mathbf{B}_1 D_1 + \mathbf{B}_2 D_2$$

$$\mathbf{C} = \mathbf{C}_1 D_1 + \mathbf{C}_2 D_2$$

$$\mathbf{E} = \mathbf{E}_1 D_1 + \mathbf{E}_2 D_2$$

$$\mathbf{F} = (\mathbf{A}_1 - \mathbf{A}_2)\mathbf{X} + (\mathbf{B}_1 - \mathbf{B}_2)\mathbf{U}$$

$$\mathbf{G} = (\mathbf{C}_1 - \mathbf{C}_2)\mathbf{X} + (\mathbf{E}_1 - \mathbf{E}_2)\mathbf{U}$$

$$\text{A.C.} \begin{cases} \frac{d\hat{i}_L}{dt} = -\left(\frac{r_L + R//r_C}{L}\right)\hat{i}_L + \frac{1}{L}\left(\frac{R}{R+r_C}\right)\hat{v}_C + \left(\frac{D}{L}\right)\hat{v}_i + \left(\frac{V_i}{L}\right)\hat{d} \\ \frac{d\hat{v}_C}{dt} = -\frac{1}{C}\left(\frac{R}{R+r_C}\right)\hat{i}_L - \frac{1}{L}\left(\frac{1}{R+r_C}\right)\hat{v}_C \\ \hat{v}_o = (R//r_C)\hat{i}_L + \left(\frac{R}{R+r_C}\right)\hat{v}_C \\ \hat{i}_s = D\hat{i}_L + I_L\hat{d} \end{cases}$$

Comments:

1. AC model gives small signal information.
2. AC model parameter value depends on dc operating point.

27/45

Time-to-Frequency Transform

Step 5. Transform ac state-space model into frequency domain (Laplace transform, s-domain).

$$\frac{d}{dt}\hat{x} = \mathbf{A}\hat{x} + \mathbf{B}\hat{u} + \mathbf{F}\hat{d}$$


$$\hat{y} = \mathbf{C}\hat{x} + \mathbf{E}\hat{u} + \mathbf{G}\hat{d}$$

In the following, the hat above the variables will be neglected for simplicity. The small signal (or ac term) of a variable is denoted using lower case letter. Thus, the dynamic equation of a PWM dc-dc converter can be represented as:

$$\frac{d}{dt}\mathbf{x} = \mathbf{A}\mathbf{x} + \mathbf{B}\mathbf{u} + \mathbf{F}d$$

$$\mathbf{y} = \mathbf{C}\mathbf{x} + \mathbf{E}\mathbf{u} + \mathbf{G}d$$

28/45

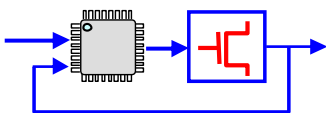

Time-to-Frequency Transform

Take Laplace transform:

$$s\mathbf{x}(s) = \mathbf{A}\mathbf{x}(s) + \mathbf{B}\mathbf{u}(s) + \mathbf{F}d(s)$$

$$\mathbf{y}(s) = \mathbf{C}\mathbf{x}(s) + \mathbf{E}\mathbf{u}(s) + \mathbf{G}d(s)$$

$$\mathbf{x}(s) = (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B}\mathbf{u}(s) + (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{F}d(s)$$

$$= \mathbf{H}_u(s)\mathbf{u}(s) + \mathbf{H}_d(s)d(s)$$

$$\mathbf{H}_u(s) = (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B}$$

$$\mathbf{H}_d(s) = (s\mathbf{I} - \mathbf{A})^{-1}\mathbf{F}d(s)$$

$$\mathbf{y}(s) = [\mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B} + \mathbf{E}]\mathbf{u}(s) + [\mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{F} + \mathbf{G}]d(s)$$

$$= \mathbf{G}_u(s)\mathbf{u}(s) + \mathbf{G}_d(s)d(s)$$

$$\mathbf{G}_u(s) = \mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B} + \mathbf{E} \Rightarrow \mathbf{G}_u(s) = \mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B} + \mathbf{E} = \begin{bmatrix} G_{u11}(s) & G_{u12}(s) \\ G_{u21}(s) & G_{u22}(s) \end{bmatrix}$$

$$\mathbf{G}_d(s) = \mathbf{C}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{F} + \mathbf{G}$$

29/45

State-Space Average Modeling: Transfer Functions

Interpretation of the transfer function matrix

Input-to-output voltage gain (audio susceptibility)

Output impedance

Control-to-output voltage gain


Input Admittance


Load-to-line current gain

Control-to-input current gain

$$\begin{bmatrix} v_o \\ i_i \end{bmatrix} = \begin{bmatrix} G_{u11}(s) & G_{u12}(s) \\ G_{u21}(s) & G_{u22}(s) \end{bmatrix} \begin{bmatrix} v_i \\ i_d \end{bmatrix} + \begin{bmatrix} G_{d1}(s) \\ G_{d2}(s) \end{bmatrix} d$$

30/45

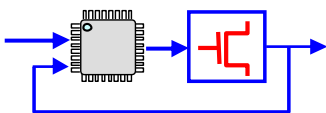

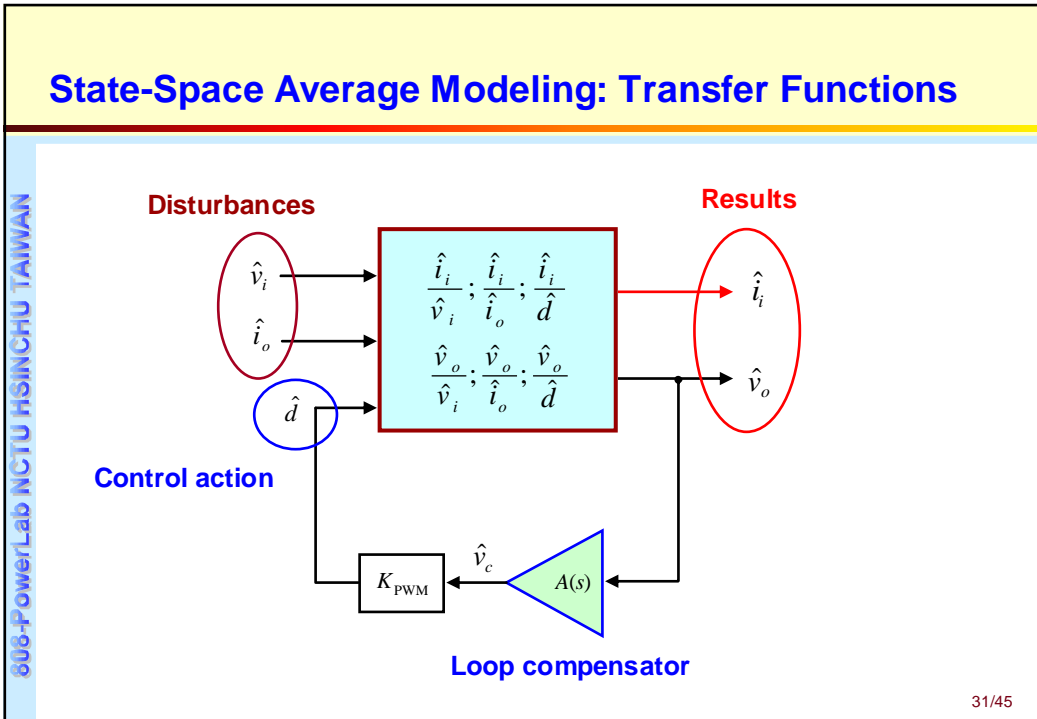


State-Space Averaging: Time-to-Frequency Transform

$$\frac{\hat{v}_o(s)}{\hat{d}(s)} = V_i \left[\frac{1 + s r_c C}{1 + s \left(r_c C + [R // r_L] C + \frac{L}{R + r_L} \right) + s^2 L C \left(\frac{R + r_c}{R + r_c + r_L} \right)} \right]$$

$$\frac{\hat{v}_o(s)}{\hat{v}_i(s)} = D \left[\frac{1 + s r_c C}{1 + s \left(r_c C + [R // r_L] C + \frac{L}{R + r_L} \right) + s^2 L C \left(\frac{R + r_c}{R + r_c + r_L} \right)} \right]$$

$$Z_o(s) = \left. \frac{v_o(s)}{i_d(s)} \right|_{\substack{d=0 \\ v_i=0}} = G_{m2}(s)$$

32/45

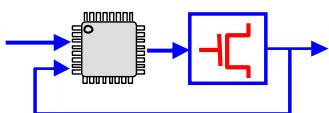

State-Space Averaging: Time-to-Frequency Transform

Note: In most conditions, because $R \gg (r_L + r_C)$, the above equations can be approximated as

$$\frac{\hat{v}_o(s)}{\hat{d}(s)} = V_i \left[\frac{1 + sr_C C}{1 + s \left(\frac{L}{R} + (r_C + r_L)C \right) + s^2 LC} \right] \quad \frac{\hat{v}_o(s)}{\hat{v}_i(s)} = D \left[\frac{1 + sr_C C}{1 + s \left(\frac{L}{R} + (r_C + r_L)C \right) + s^2 LC} \right]$$

$$\frac{\hat{v}_o(s)}{\hat{d}(s)} = V_i \left[\frac{1 + sr_C C}{1 + s \left(\frac{L}{R} + (r_C + r_L)C \right) + s^2 LC} \right]$$

$$\frac{\hat{v}_o(s)}{\hat{d}(s)} = V_i \frac{1 + sr_C C}{\Delta s / \omega_o^2}$$

$$\Delta s = s^2 + \frac{\omega_b}{Q} s + \omega_o^2$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{1}{\omega_o} \frac{1}{\frac{L}{R} + (r_L + r_C)C}$$

33/45

State-Space Average Modeling


The small signal control-to-output $\frac{\hat{v}_o(s)}{\hat{d}(s)}$, and line-to-output $\frac{\hat{v}_o(s)}{\hat{v}_i(s)}$ are transfer functions of two poles and one zero

$$K \frac{(s + z_1)}{(s + p_1)(s + p_2)}$$

with its parameters depending upon component values and operating point. p_1, p_2 can be complex poles or real poles. But p_1, p_2 and z_1 all lie on LHP.

Note: The equivalent series resistance of the capacitor will introduce a LHP zero.

34/45

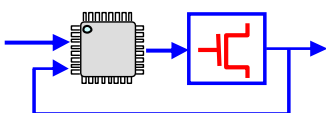

State-Space Averaging: Output Impedance

Output Impedance: $Z_o(s) = \left. \frac{v_o(s)}{i_d(s)} \right|_{d=0, u=0} = \mathbf{c}(s\mathbf{I} - \mathbf{A})^{-1}\mathbf{B} + \mathbf{d}\mathbf{u}$



$$\frac{\hat{v}_o(s)}{\hat{i}_d(s)} = R \frac{1 + \frac{s}{\omega_1 Q_1} + (\frac{s}{\omega_1})^2}{\Delta s / \omega_o^2}$$


$$\Delta s = s^2 + \frac{\omega_o}{Q} s + \omega_o^2$$

$$\omega_o = \frac{1}{\sqrt{LC}}, \quad Q = \frac{1}{\omega_o} \frac{1}{\frac{L}{R} + (r_L + r_C)C}$$


$$\omega_1 = \frac{1}{\sqrt{LC}} \sqrt{\frac{r_L}{r_C}}; \quad Q_1 = \frac{1}{\omega_1} \frac{1}{\frac{L}{R} + r_C C}$$

35/45

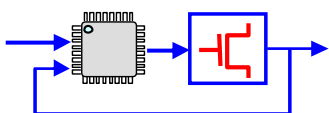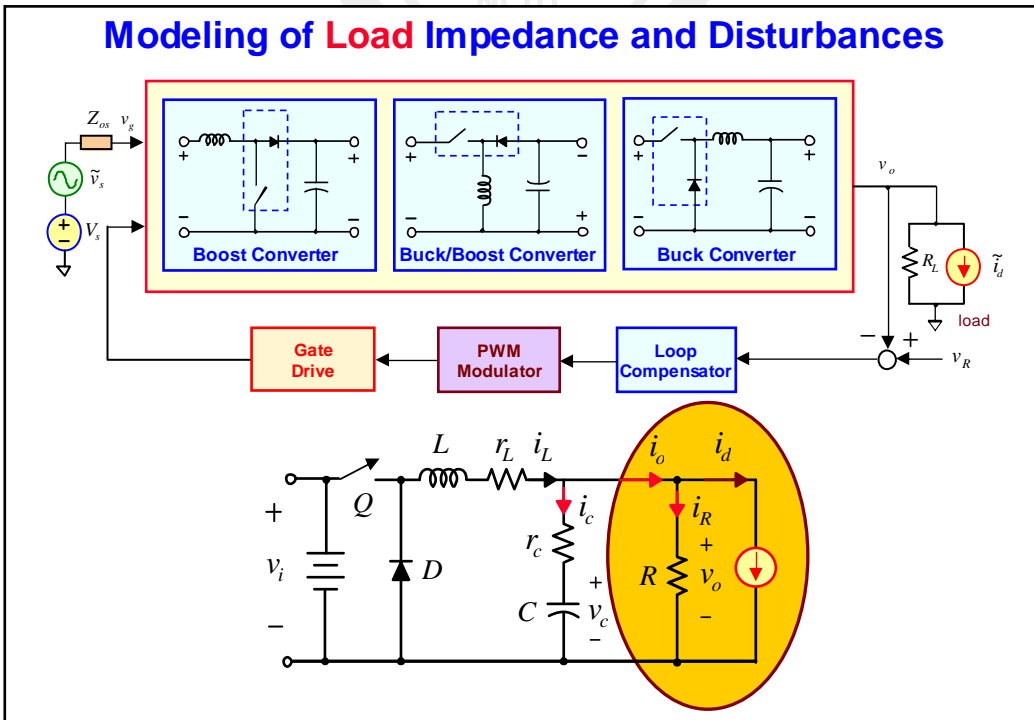


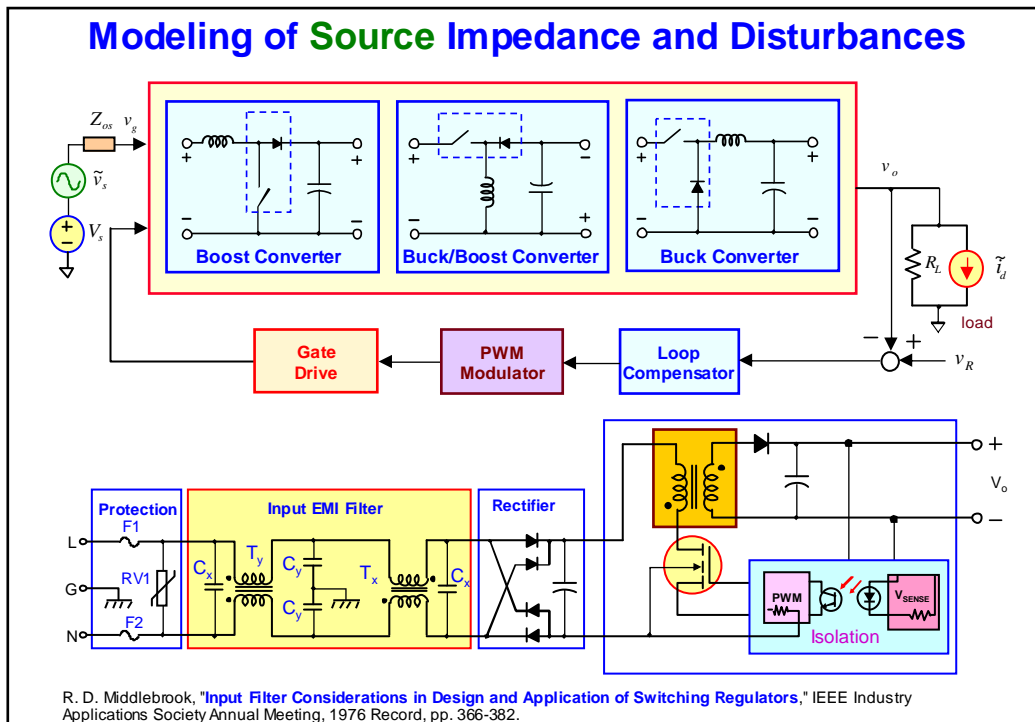


Dynamic Responses for Step Load Changes

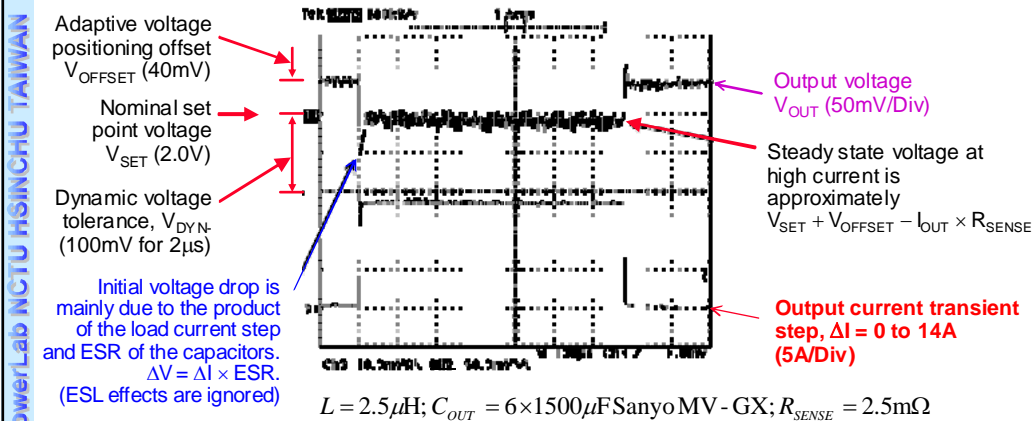


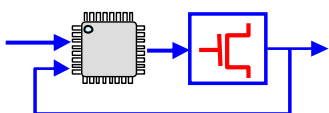Intel: VRM (Voltage Regulator Module) and Enterprise Voltage Regulator-Down (EVRD) 11.0 Design Guidelines, Nov. 2006.



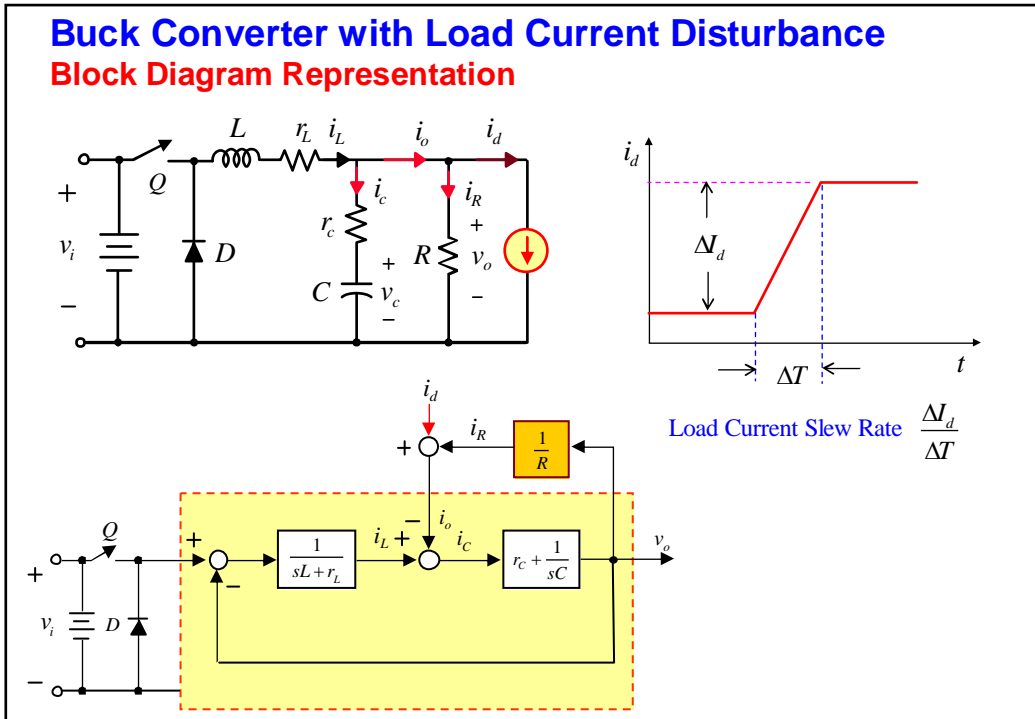

Control-to-Output Transfer Functions DC-DC Converters in CCM Operating Mode		
	<p style="text-align: center;">■ Buck</p> $\frac{\hat{v}_o(s)}{\hat{d}(s)} = V_i \frac{1+r_cCs}{\left(\frac{s}{\omega_o}\right)^2 + \frac{1}{\omega_o Q}s + 1}$	$\omega_o = \frac{1}{\sqrt{LC}}$ $Q = \frac{1}{\omega_o} \frac{1}{\frac{L}{R} + (r_L + r_c)C}$
	<p style="text-align: center;">■ Boost</p> $\frac{\hat{v}_o(s)}{\hat{d}(s)} = \frac{V_i}{D^2} \frac{(1+r_cCs)(1-sL/(D^2R))}{\left(\frac{s}{\omega_o}\right)^2 + \frac{1}{\omega_o Q}s + 1}$	$\omega_o = \frac{D}{\sqrt{LC}}$ $Q = \frac{D}{\omega_o} \frac{1}{\frac{L}{DR} + \frac{r_cC}{D} + r_cC}$
	<p style="text-align: center;">■ Buck/Boost</p> $\frac{\hat{v}_o(s)}{\hat{d}(s)} = \frac{V_i}{D^2} \frac{(1+r_cCs)(1-sDL/(D^2R))}{\left(\frac{s}{\omega_o}\right)^2 + \frac{1}{\omega_o Q}s + 1}$	$\omega_o = \frac{D}{\sqrt{LC}}$ $Q = \frac{D}{\omega_o} \frac{1}{\frac{L}{(D)^2R} + \left(\frac{r_c}{D} + \frac{r_L}{(D)^2}\right)C}$

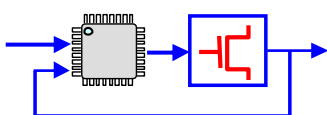

Transfer Functions of Buck Converters

Transfer Function	Transfer Function
$\frac{\hat{v}_o(s)}{\hat{d}(s)} = V_i \frac{1 + r_c C s}{\Delta s / \omega_o^2} = \frac{F_{D1}}{\Delta}$	$\frac{\hat{i}_d(s)}{\hat{d}(s)} = \frac{V_i}{r_L} \frac{1 + r_c C s}{\Delta s / \omega_o^2} = \frac{F_{D2}}{\Delta}$
$\frac{\hat{v}_o(s)}{\hat{v}_i(s)} = D \frac{1 + r_c C s}{\Delta s / \omega_o^2} = \frac{F_{U11}}{\Delta}$	$\frac{\hat{i}_L(s)}{\hat{v}_i(s)} = \frac{D}{R} \frac{1 + R C s}{\Delta s / \omega_o^2} = \frac{F_{U21}}{\Delta}$
$\frac{\hat{v}_o(s)}{\hat{i}_d(s)} = R_{eq} \frac{1 + \frac{s}{\omega_z} + (\frac{s}{\omega_a})^2}{\Delta s / \omega_o^2} = \frac{F_{U12}}{\Delta}$	$\frac{\hat{i}_L(s)}{\hat{i}_d(s)} = -\frac{1 + r_c C s}{\Delta s / \omega_o^2} = \frac{F_{U22}}{\Delta}$

$$\Delta s = s^2 + \frac{\omega_o}{Q} s + \omega_o^2, \quad R_{eq} = r_L$$

$$\omega_o = \frac{1}{\sqrt{LC}}, \quad Q = \frac{1}{\omega_o} \frac{1}{\frac{L}{R} + (r_L + r_c)C}$$

$$\omega_1 = \frac{1}{\sqrt{LC}} \sqrt{\frac{r_L}{r_c}}; \quad Q_1 = \frac{1}{\omega_1} \frac{1}{\frac{L}{r_c} + r_L C}$$

41/45

Transfer Functions of Boost Converters

Transfer Function	Transfer Function
$\frac{\hat{v}_o(s)}{\hat{d}(s)} = \frac{V_i}{(D')^2} \frac{(1 + \frac{s}{\omega_z})(1 - \frac{s}{\omega_a})}{\Delta s / \omega_o^2} = \frac{F_{D1}}{\Delta}$	$\frac{\hat{i}_d(s)}{\hat{d}(s)} = \frac{2V_i}{(D')^3 R} \frac{1 + \frac{RC}{2}}{\Delta s / \omega_o^2} = \frac{F_{D2}}{\Delta}$
$\frac{\hat{v}_o(s)}{\hat{v}_i(s)} = \frac{1}{D'} \frac{1}{\Delta s / \omega_o^2} = \frac{F_{U11}}{\Delta}$	$\frac{\hat{i}_L(s)}{\hat{v}_i(s)} = \frac{2V_i}{(D')^3 R} \frac{1 + RC}{\Delta s / \omega_o^2} = \frac{F_{U21}}{\Delta}$
$\frac{\hat{v}_o(s)}{\hat{i}_d(s)} = R_{eq} \frac{1 + \frac{s}{\omega_z} + (\frac{s}{\omega_a})^2}{\Delta s / \omega_o^2} = \frac{F_{U12}}{\Delta}$	$\frac{\hat{i}_L(s)}{\hat{i}_d(s)} = -\frac{1}{D'} \frac{1 + r_c C s}{\Delta s / \omega_o^2} = \frac{F_{U22}}{\Delta}$


$$\Delta s = s^2 + \frac{\omega_o}{Q} s + \omega_o^2, \quad Q = \frac{D'}{\omega_o} \frac{1}{\frac{L}{D'R} + \frac{r_L C}{D'} + D' r_c C}$$

$$\omega_o = \frac{D'}{\sqrt{LC}}$$

$$\omega_1 = \frac{D'}{\sqrt{LC}} \sqrt{\frac{R_{eq}}{r_c}}; \quad Q_1 = \frac{1}{\omega_1} \frac{1}{(\frac{L}{D'^2 R_{eq}} + r_c C)}$$

$$\omega_z = \frac{1}{r_c C}; \quad \omega_a = \frac{(D')^2 R}{L} \quad R_{eq} = \frac{r_L}{D'^2} \frac{D'}{r_c}$$

42/45

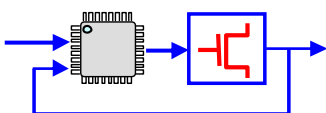

Transfer Functions of Buck/Boost Converters

Transfer Function	Transfer Function
$\frac{\hat{v}_o(s)}{\hat{d}(s)} = \frac{V_i}{(D)^2} \frac{(1 + \frac{s}{\omega_z})(1 - \frac{s}{\omega_a})}{\Delta s / \omega_o^2} = \frac{F_{U1}}{\Delta}$	$\frac{\hat{i}_l(s)}{\hat{d}(s)} = -\frac{V_i}{(D)^2} \frac{1 + RCs}{R \Delta s / \omega_o^2} = \frac{F_{I1}}{\Delta}$
$\frac{\hat{v}_o(s)}{\hat{v}_i(s)} = \frac{D}{D} \frac{(1 + r_c Cs)}{\Delta s / \omega_o^2} = \frac{F_{U11}}{\Delta}$	$\frac{\hat{i}_l(s)}{\hat{v}_i(s)} = -\frac{D}{(D)^2} \frac{1 + RCs}{R \Delta s / \omega_o^2} = \frac{F_{I11}}{\Delta}$
$\frac{\hat{v}_o(s)}{\hat{i}_d(s)} = R_{eq} \frac{1 + \frac{s}{\omega_o Q} + (\frac{s}{\omega_1})^2}{\Delta s / \omega_o^2} = \frac{F_{U12}}{\Delta}$	$\frac{\hat{i}_l(s)}{\hat{i}_d(s)} = -\frac{1}{D} \frac{1 + r_c Cs}{\Delta s / \omega_o^2} = \frac{F_{I12}}{\Delta}$

$$\Delta s = s^2 + \frac{\omega_o}{Q}s + \omega_o^2$$

$$\omega_o = \frac{D}{\sqrt{LC}}$$

$$Q = \frac{D}{\omega_o} \frac{1}{\frac{L}{(D)^2 R} + (\frac{r_c}{D} + \frac{r_l}{(D)^2})C}$$


$$\omega_z = \frac{1}{r_c C}, \quad \omega_a = \frac{(D)^2 R}{DL}; \quad R_{eq} = \frac{r_l}{(D)^2} + \frac{D}{D} r_c$$

$$\omega_1 = \omega_o \sqrt{\frac{R_{eq}}{r_c}}$$

$$Q_1 = \frac{1}{\omega_1} \frac{1}{\frac{L}{D^2 R_{eq}} + r_c C}$$

43/45

Q-factor of Buck Converter

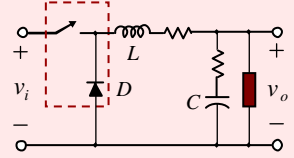

• Buck

$$\frac{\hat{v}_o(s)}{\hat{d}(s)} = V_i \frac{1 + r_c Cs}{(\frac{s}{\omega_o})^2 + \frac{1}{\omega_o Q} s + 1}$$

$$\omega_o = \frac{1}{\sqrt{LC}}$$


$$Q = \frac{1}{\omega_o} \frac{1}{\frac{L}{R} + (r_l + r_c)C}$$

$$\rightarrow Q = \frac{1}{\omega_o} \frac{1}{\frac{L}{R} + (r_l + r_c)C} = \frac{1}{\frac{1}{\sqrt{LC}} \frac{L}{R} + (r_l + r_c)C} = \frac{1}{\frac{1}{R} \sqrt{\frac{L}{C}} + (r_l + r_c) \sqrt{\frac{C}{L}}} = \frac{1}{\frac{Z_o}{R} + \frac{r_l + r_c}{Z_o}}$$

$$Q = \frac{1}{\omega_o} \frac{1}{\frac{L}{R} + (r_l + r_c)C} = \frac{1}{\frac{Z_o}{R} + \frac{r_l + r_c}{Z_o}}$$

$$\rightarrow Q = \frac{1}{\omega_o} \frac{1}{\frac{L}{R} + (r_l + r_c)C} \approx \frac{\sqrt{LC}}{\frac{L}{R}} = \frac{R}{\sqrt{L/C}}$$

44/45

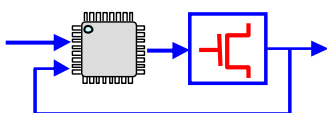

808-PowerLab NCTU HSINCHU TAIWAN

Summary: Buck Converters at CCM

Transfer Function	Transfer Function
$\frac{\hat{v}_o(s)}{\hat{d}(s)} = V_i \frac{1 + r_c Cs}{\Delta s / \omega_o^2} = \frac{F_{D1}}{\Delta}$	$\frac{\hat{i}_L(s)}{\hat{d}(s)} = \frac{V_i}{r_L} \frac{1 + r_c Cs}{\Delta s / \omega_o^2} = \frac{F_{D2}}{\Delta}$
$\frac{\hat{v}_o(s)}{\hat{v}_i(s)} = D \frac{1 + r_c Cs}{\Delta s / \omega_o^2} = \frac{F_{U11}}{\Delta}$	$\frac{\hat{i}_L(s)}{\hat{v}_i(s)} = \frac{D}{R} \frac{1 + RCs}{\Delta s / \omega_o^2} = \frac{F_{U21}}{\Delta}$
$\frac{\hat{v}_o(s)}{\hat{i}_d(s)} = R_{eq} \frac{1 + \frac{s}{\omega_1 Q_1} + (\frac{s}{\omega_1})^2}{\Delta s / \omega_o^2} = \frac{F_{U12}}{\Delta}$	$\frac{\hat{i}_L(s)}{\hat{i}_d(s)} = -\frac{1 + r_c Cs}{\Delta s / \omega_o^2} = \frac{F_{U22}}{\Delta}$

Switch-ON Period

$\dot{\mathbf{x}} = \mathbf{A}_1 \mathbf{x} + \mathbf{B}_1 \mathbf{u}$
 $\mathbf{y} = \mathbf{C}_1 \mathbf{x} + \mathbf{E}_1 \mathbf{u}$

$\times d_1 +$

Switch-OFF Period

$\dot{\mathbf{x}} = \mathbf{A}_2 \mathbf{x} + \mathbf{B}_2 \mathbf{u}$
 $\mathbf{y} = \mathbf{C}_2 \mathbf{x} + \mathbf{E}_2 \mathbf{u}$

$\times d_2$

$\mathbf{x} = \mathbf{A}\mathbf{x} + \mathbf{B}\mathbf{u}$
 $\mathbf{y} = \mathbf{C}\mathbf{x} + \mathbf{D}\mathbf{u}$
 where
 $\mathbf{A} = \mathbf{A}_1 d_1 + \mathbf{A}_2 d_2$
 $\mathbf{B} = \mathbf{B}_1 d_1 + \mathbf{B}_2 d_2$
 $\mathbf{C} = \mathbf{C}_1 d_1 + \mathbf{C}_2 d_2$
 $\mathbf{E} = \mathbf{E}_1 d_1 + \mathbf{E}_2 d_2$

averaging by using state duty ratio weighting

45/45

808-PowerLab NCTU HSINCHU TAIWAN

808-PowerLab. NCTU
 Power Electronic Systems & Chips Lab., NCTU, Taiwan

Any Questions ???

Questions inspire effective learning!

學習的關鍵

● 記筆記

● 問問題

電力電子系統與晶片實驗室

Power Electronic Systems & Chips Lab.

交通大學 • 電機與控制工程研究所

46/45

