



台灣新竹·交通大學·電機與控制工程研究所·808實驗室  
電力電子系統晶片、數位電源、DSP控制、馬達與伺服控制  
Lab-808: Power Electronic Systems & Chips Lab., NCTU, Taiwan  
<http://pemclab.cn.nctu.edu.tw/>

## PWM Switch Model

鄒應嶼 教授

國立交通大學 電機與控制工程研究所

2009年5月22日



Lab808: 電力電子系統與晶片實驗室  
Power Electronic Systems & Chips, NCTU, TAIWAN  
台灣新竹·交通大學·電機與控制工程研究所

808-PowerLab NCTU HSINCHU TAIWAN


1/25

## PWM Switch Model

- Introduction
- PWM Switch and its Invariant Properties
- CCM Analysis
  - ◆ DC and Small-Signal Model of PWM Switch
  - ◆ PWM Switch Model of Buck Converters
  - ◆ PWM Switch Model of Boost Converters
  - ◆ PWM Switch Model of Buck/Boost Converters
  - ◆ PWM Switch Model of Cuk Converters
  - ◆ Analysis of PWM Converters
  - ◆ Right-half Plane Zero of the Converters
  - ◆ PWM Switch Model Including Storage-Time Modulation
- DCM Analysis
  - ◆ DC and Small Model of PWM Switch
  - ◆ Analysis of PWM Converters
  - ◆ Zero of Control-to-Output Transfer Function in DCM

808-PowerLab NCTU HSINCHU TAIWAN

2/25

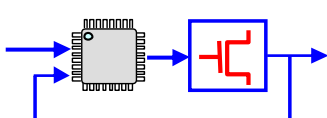


**PWM Switch Model (1990)**

808-PowerLab NCTU HSINCHU TAIWAN

**□ PWM Switch Method**


[1] V. Vorperian, "Simplified Analysis of PWM Converters Using Model of PWM Switch Part I: **Continuous Conduction Mode**," *IEEE Trans. on Aero. and Elec. Sys.*, vol. 26, no. 3, pp. 490-496, May 1990.

[2] V. Vorperian, "Simplified Analysis of PWM Converters Using Model of PWM Switch Part II: **Discontinuous Conduction Mode**," *IEEE Trans. on Aero. and Electron. Sys.*, vol. 26, no. 3, pp. 497-505, May 1990.



**Fast Analytical Techniques for Electrical and Electronic Circuits,**  
**V. Vorperian, Cambridge Press, 2004.**


1. Introduction
2. Transfer functions
3. The extra element theorem
4. The N-extra element theorem
5. Electronic negative feedback
6. High-frequency and microwave circuits
7. Passive filters
8. **PWM switching dc-to-dc converters**




3/25

**Pulse-Width Modulator**

808-PowerLab NCTU HSINCHU TAIWAN

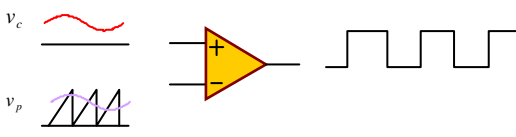

For natural sampling,

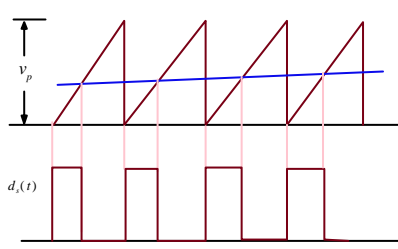


$$D = \frac{T_{ON}}{T_S} = \frac{v_c}{v_p}$$

$$\hat{d}(s) = K_m v_c(s)$$

$$K_m = \frac{1}{v_p} = \text{constant}$$

4/25

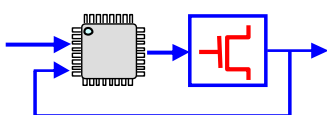

### PWM Switch Model

Instantaneous value

(active)  $\tilde{i}_a(t)$   $d$   $\tilde{i}_c(t)$  (common)  
 $\tilde{v}_{ap}(t)$   $1-d$   $\tilde{v}_{cp}(t)$   
 (passive)  $p$

**PWM Switch Modeling**

- [1] V. Vorperian, R. Tymerski, and F.C.Y. Lee, "Equivalent circuit models for resonant and PWM switches," *IEEE Transactions on Power Electronics*, vol. 4, no. 2, pp. 205-214, Apr 1989.
- [1] V. Vorperian, "Simplified Analysis of PWM Converters Using Model of PWM Switch Part I: Continuous Conduction Mode," *IEEE Trans. on Aero. and Electron. Sys.*, vol. 26, no. 3, pp. 490-496, May 1990.
- [2] V. Vorperian, "Simplified Analysis of PWM Converters Using Model of PWM Switch Part II: Discontinuous Conduction Mode," *IEEE Trans. on Aero. and Electron. Sys.*, vol. 26, no. 3, pp. 497-505, May 1990.
- [3] E. Van Dijk, J. N. Spruijt, D. M. O'Sullivan, and J. B. Klaassens, "PWM-switch modeling of DC-DC converters," *IEEE Transactions on Power Electronics*, vol. 10, no. 6, pp. 659-665, Nov 1995.

5/25

### Modeling of the Switch

$i_a = Di_c$   
 $\tilde{i}_c(t)$   $\tilde{i}_a(t)$


$v_{cp} = Dv_{ap}$   
 $\tilde{v}_{ap}(t)$   $\tilde{v}_{cp}(t)$

Note:  $i_a$  denotes the average value of  $\tilde{i}_a(t)$

During a PWM switching interval:

$$\tilde{i}_a(t) = \begin{cases} \tilde{i}_c(t), & 0 \leq t \leq DT_s \\ 0, & DT_s \leq t \leq T_s \end{cases} \quad \tilde{v}_{cp}(t) = \begin{cases} \tilde{v}_{ap}(t), & 0 \leq t \leq DT_s \\ 0, & DT_s \leq t \leq T_s \end{cases}$$

6/25

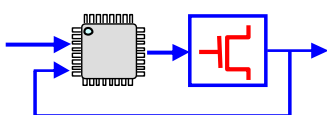

808-PowerLab NCTU HSINCHU TAIWAN

## Small-Signal Perturbation

Make a small-signal perturbation at a DC operating point

$$d = D + \hat{d} \quad \begin{matrix} i_a = I_a + \hat{i}_a \\ i_c = I_c + \hat{i}_c \end{matrix} \quad \begin{matrix} v_{cp} = V_{cp} + \hat{v}_{cp} \\ v_{ap} = V_{ap} + \hat{v}_{ap} \end{matrix}$$

We can obtain

$i_a = D\hat{i}_c$

➔

$$i_a = d\hat{i}_c$$

$$I_a + \hat{i}_a = (D + \hat{d})(I_c + \hat{i}_c)$$

$$I_a + \hat{i}_a = DI_c + I_c\hat{d} + D\hat{i}_c + \hat{d}\hat{i}_c$$

$v_{cp} = DV_{ap}$

➔

$$v_{cp} = dv_{ap}$$

$$V_{cp} + \hat{v}_{cp} = (D + \hat{d})(V_{ap} + \hat{v}_{ap})$$

$$V_{cp} + \hat{v}_{cp} = DV_{ap} + V_{ap}\hat{d} + D\hat{v}_{ap} + \hat{d}\hat{v}_{ap}$$

7/25

808-PowerLab NCTU HSINCHU TAIWAN

## DC and AC Analysis

For dc analysis, eliminate all small signal perturbation terms, we can get its equivalent dc model.

$$I_a = DI_c$$


$$V_{cp} = DV_{ap}$$

For ac analysis, set all dc terms to zero and neglect second order nonlinear terms, we can get its equivalent small-signal ac model.

$$\hat{i}_a = I_c\hat{d} + D\hat{i}_c$$

$$\hat{v}_{cp} = V_{ap}\hat{d} + D\hat{v}_{ap}$$

8/25

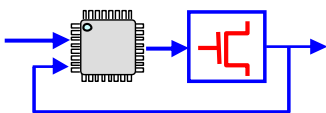

### PWM Switch Model

**DC Model:**

$$\begin{cases} I_a = DI_c \\ V_{cp} = DV_{ap} \end{cases}$$

**AC Model:**

$$\begin{cases} \hat{i}_a = D\hat{i}_c + I_c\hat{d} \\ \hat{v}_{cp} = D\hat{v}_{ap} + V_{ap}\hat{d} \end{cases}$$


9/25

### DC Analysis of a Buck Converter

**DC Analysis**

$$\frac{V_o}{V_i} = D \cdot \left( \frac{R}{R+r_L} \right)$$

10/25

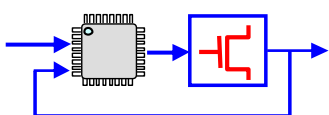

808-PowerLab NCTU HSINCHU TAIWAN

### AC Analysis of a Buck Converter

Small-signal equivalent circuit model of the buck converter.

*Note:*  
 In the following, the hat above the small signal variables are neglected for simplicity.


11/25

808-PowerLab NCTU HSINCHU TAIWAN

### AC Analysis: Control-to-Output Transfer Function

Short the unrelated voltage source and open the unrelated current source

12/25

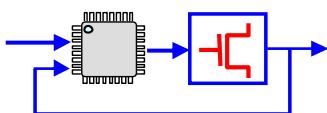

### AC Analysis: Control-to-Output Transfer Function

808-PowerLab NCTU HSINCHU TAIWAN

$$v_{cp} = \frac{V_i}{D} \cdot D$$

$$v_o = v_{cp} \frac{R // (r_c + 1/sC)}{(r_L + sL) + R // (r_c + 1/sC)}$$


$$= V_i d \frac{R(1 + sr_c C)}{s^2(R + r_c)LC + s(r_L r_c C + r_L RC + L + r_c RC) + (R + r_L)}$$

$$G_d(s) = \frac{v_o(s)}{d(s)} = V_i \frac{R(1 + sr_c C)}{s^2 RLC + s(r_L r_c C + L + r_L RC + r_c RC) + (R + r_L)}$$

if  $r_L \ll R$  and  $r_L r_c$  can be neglected, the above eq. can be simplified as:

$$G_d(s) = \frac{v_o(s)}{d(s)} = \frac{V_i}{LC} \cdot \frac{1 + sr_c C}{s^2 + s\left(\frac{1}{RC} + \frac{r_L + r_c}{L}\right) + \frac{1}{LC}}$$

13/25

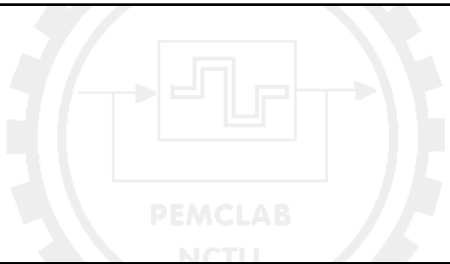


### AC Analysis: Line-to-Output Transfer Function

808-PowerLab NCTU HSINCHU TAIWAN

$$R // (r_c + 1/sC) = \frac{R(r_c + 1/sC)}{R + r_c + 1/sC}$$

14/25

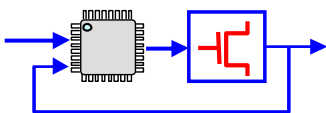

### AC Analysis: Line-to-Output Transfer Function

$v_{cp} = v_i D$

$$v_o = v_{cp} \frac{R/(r_c + 1/sC)}{(r_L + sL) + R/(r_c + 1/sC)} = v_i D \frac{\frac{R(r_c + 1/sC)}{R + r_c + 1/sC}}{(r_L + sL) + \frac{R(r_c + 1/sC)}{R + r_c + 1/sC}}$$

$$= v_i D \frac{R(r_c + 1/sC)}{(r_L + sL)(R + r_c + 1/sC) + R(r_c + 1/sC)} = v_i D \frac{R(1 + sr_c C)}{(r_L + sL)(sRC + sr_c C + 1) + R(sr_c C + 1)}$$

$$= v_i D \frac{R(1 + sr_c C)}{s^2(R + r_c)LC + s(r_L r_c C + r_L RC + L + r_c RC) + (R + r_L)}$$

$$G_v(s) = \frac{v_o(s)}{v_i(s)} = D \frac{R(1 + sr_c C)}{s^2 RLC + s(r_L r_c C + L + r_L RC + r_c RC) + (R + r_L)}$$


if  $r_L \ll R$  and  $r_L r_c C$  can be neglected, the above equation can be simplified as:

$$G_v(s) = \frac{v_o(s)}{v_i(s)} = \frac{D}{LC} \cdot \frac{1 + sr_c C}{s^2 + s\left(\frac{1}{RC} + \frac{r_L + r_c}{L}\right) + \frac{1}{LC}}$$

15/25

### AC Analysis: Disturbance-to-Output Transfer Function

16/25

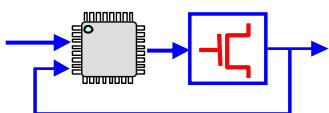



## AC Analysis: Disturbance-to-Output Transfer Function

$$\begin{aligned} \frac{v_o}{i_d} &= R // (r_c + 1/sC) // (r_L + sL) = \frac{R(r_c + 1/sC)}{R + r_c + 1/sC} // (r_L + sL) \\ &= \frac{\frac{R(r_c + 1/sC)}{R + r_c + 1/sC} (r_L + sL)}{\frac{R(r_c + 1/sC)}{R + r_c + 1/sC} + r_L + sL} = \frac{R(r_c + 1/sC)(r_L + sL)}{R(r_c + 1/sC) + (R + r_c + 1/sC)(r_L + sL)} \\ &= \frac{R(sr_c C + 1)(r_L + sL)}{R(sr_c C + 1) + (sRC + sr_c C + 1)(r_L + sL)} = \frac{R[s^2 r_c LC + sr_L r_c C + sL + r_L]}{sr_c RC + R + (sRC + sr_c C + 1)(r_L + sL)} \\ &= \frac{R[s^2 r_c LC + sr_L r_c C + sL + r_L]}{sr_c RC + R + s^2 RLC + s^2 r_c LC + sr_c r_L C + sr_L RC + sL + r_L} \\ \\ \frac{v_o}{i_d} &= \frac{R[s^2 r_c LC + s(L + r_L r_c C) + r_L]}{s^2 (R + r_c) LC + s[L + (r_c + r_L)RC + r_c r_L C] + (R + r_L)} \end{aligned}$$

17/25

## AC Analysis: Disturbance-to-Output Transfer Function


if  $r_L \ll R$  and  $r_L r_c$  can be neglected, the above equation can be simplified as:

$$\begin{aligned} Z_o(s) = \frac{v_o(s)}{i_d(s)} &= \frac{R[s^2 r_c LC + sL + r_L]}{s^2 RLC + s[L + (r_c + r_L)RC] + R} \\ &= \frac{s^2 r_c LC + sL + r_L}{s^2 LC + s\left[\frac{L}{R} + (r_c + r_L)C\right] + 1} = \frac{s^2 r_c + s\frac{1}{C} + \frac{r_L}{LC}}{s^2 + s\left[\frac{1}{RC} + \frac{r_c + r_L}{L}\right] + \frac{1}{LC}} \end{aligned}$$

The Output Impedance of a Buck Converter is:

$$Z_o(s) = \frac{v_o(s)}{i_d(s)} = \frac{s^2 r_c + s\frac{1}{C} + \frac{r_L}{LC}}{s^2 + s\left[\frac{1}{RC} + \frac{r_c + r_L}{L}\right] + \frac{1}{LC}}$$

18/25

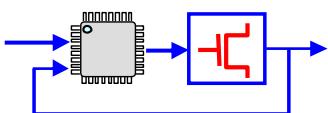

## AC Analysis: Disturbance-to-Output Transfer Function

$$Z_o(s) = \frac{v_o(s)}{i_d(s)} = \frac{s^2 r_c + s \frac{1}{C} + \frac{r_L}{LC}}{s^2 + s \left[ \frac{1}{RC} + \frac{r_c + r_L}{L} \right] + \frac{1}{LC}}$$

$$\omega_o^2 = \frac{1}{LC} \quad \Rightarrow \quad \omega = \frac{1}{\sqrt{LC}}$$

$$\frac{\omega_o}{Q} = \frac{1}{RC} + \frac{r_c + r_L}{L}$$

$$Q = \frac{1}{\omega_o} \frac{\omega_o^2}{\frac{1}{RC} + \frac{r_c + r_L}{L}} = \frac{1}{\omega_o} \frac{1}{LC \left( \frac{1}{RC} + \frac{r_c + r_L}{L} \right)} = \frac{1}{\omega_o} \frac{1}{\frac{L}{R} + (r_c + r_L)L}$$

19/25

## AC Analysis: Disturbance-to-Output Transfer Function

$$Q = \frac{1}{\omega_o} \frac{1}{\frac{L}{R} + (r_c + r_L)L}$$

$$\begin{aligned} Z_{op}(s) &= s^2 + s \left[ \frac{1}{RC} + \frac{r_c + r_L}{L} \right] + \frac{1}{LC} \\ &= s^2 + s \frac{\omega_o}{Q} + \omega_o^2 \end{aligned}$$

$$\Delta s = s^2 + s \frac{\omega_o}{Q} + \omega_o^2$$


$$\begin{aligned} Z_{oq}(s) &= s^2 r_c + s \frac{1}{C} + \frac{r_L}{LC} \\ &= \frac{r_L}{LC} \left( \frac{r_c}{r_L} LC s^2 + \frac{L}{r_L} s + 1 \right) \\ &= R_{eq} \omega_o^2 \left( \frac{1}{\omega_1^2} s^2 + \frac{1}{\omega_1 Q_1} s + 1 \right) \end{aligned}$$

$$R_{eq} = r_L$$

$$\omega_1 = \sqrt{\frac{r_L}{r_c} \frac{1}{\sqrt{LC}}}$$

$$Q_1 = \frac{1}{\omega_1} \frac{r_L}{L}$$

20/25

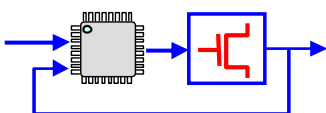

## AC Analysis: Disturbance-to-Output Transfer Function

The exact output impedance is derived as:

$$\begin{aligned} \frac{v_o}{i_d} &= \frac{R[s^2 r_c LC + s(L + r_L r_c C) + r_L]}{s^2(R + r_c)LC + s[L + (r_c + r_L)RC + r_c r_L C] + (R + r_L)} \\ &= \frac{s^2 r_c LC + s(L + r_L r_c C) + r_L}{s^2(1 + \frac{r_c}{R})LC + s\left[\frac{L}{R} + (r_c + r_L)C + r_c r_L \frac{C}{R}\right] + (1 + \frac{r_L}{R})} \\ &= \frac{s^2 r_c + s\left(\frac{1}{C} + \frac{r_L r_c}{L}\right) + \frac{r_L}{LC}}{s^2(1 + \frac{r_c}{R}) + s\left[\frac{1}{RC} + \frac{1}{L}(r_c + r_L + \frac{r_L r_c}{R})\right] + (1 + \frac{r_L}{R})\frac{1}{LC}} \end{aligned}$$

21/25

## AC Analysis: Disturbance-to-Output Transfer Function


$$\begin{aligned} Z_{oq}(s) &= s^2 r_c + s\left(\frac{1}{C} + \frac{r_L r_c}{L}\right) + \frac{r_L}{LC} = \frac{r_L}{LC} \left( \frac{r_c}{r_L} LC s^2 + \left(\frac{L}{r_L} + r_c C\right) s + 1 \right) \\ &= R_{eq} \omega_o^2 \left( \frac{1}{\omega_1^2} s^2 + \frac{1}{\omega_1 Q_1} s + 1 \right) \end{aligned}$$

$$R_{eq} = r_L$$

$$\omega_1 = \sqrt{\frac{r_L}{r_c}} \frac{1}{\sqrt{LC}}$$

$$Q_1 = \frac{1}{\omega_1} \frac{1}{\frac{L}{r_L} + r_c C}$$

22/25

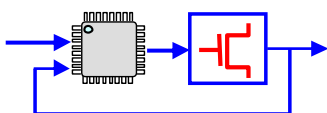

808-PowerLab NCTU HSINCHU TAIWAN

## Output Impedance of the Buck Converter

**Output Impedance of the Buck Converter:**

$$Z_o(s) = \frac{v_o(s)}{i_d(s)} = \frac{s^2 r_c + s \left( \frac{1}{C} + \frac{r_L r_c}{L} \right) + \frac{r_L}{LC}}{s^2 \left( 1 + \frac{r_c}{R} \right) + s \left[ \frac{1}{RC} + \frac{1}{L} (r_c + r_L + \frac{r_L r_c}{R}) \right] + \left( 1 + \frac{r_L}{R} \right) \frac{1}{LC}}$$


$$Z_o(s) = \frac{v_o(s)}{i_d(s)} = R_{eq} \frac{1 + \frac{s}{\omega_1 Q_1} + \left( \frac{s}{\omega_1} \right)^2}{\Delta s / \omega_o^2}$$

$$\Delta s = s^2 + \frac{\omega_o}{Q} s + \omega_o^2, \quad R_{eq} = r_L$$

$$\omega_o = \frac{1}{\sqrt{LC}}, \quad Q = \frac{1}{\omega_o} \frac{1}{\frac{L}{R} + (r_L + r_c)C}$$


$$\omega_1 = \frac{1}{\sqrt{LC}} \sqrt{\frac{r_L}{r_c}}; \quad Q_1 = \frac{1}{\omega_1} \frac{1}{\frac{L}{r_c} + r_L C}$$


23/25

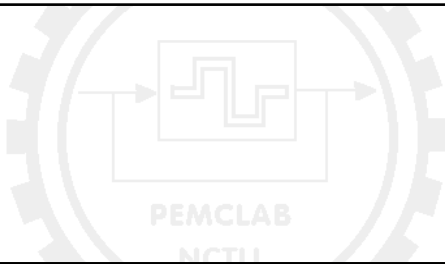



808-PowerLab NCTU HSINCHU TAIWAN

## Recommended Books: Modeling and Simulation

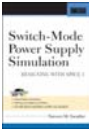- 


**Dynamic Analysis of Switching-Mode DC/DC Converters,**  
 Andre'S. Kislovski, Richard Redl, and Nathan O. Sokal,  
 Van Nostrand Reinhold, New York, 1991.
- 

**Switch-Mode Power Supply Simulation: Designing with SPICE 3**  
 Steven M. Sandler,  
 McGraw-Hill Professional; 1 edition, Nov. 11, 2005.
- 

**Switch-Mode Power Supplies - SPICE Simulations and Practical Designs,**  
 Christophe Basso,  
 McGraw-Hill, Feb. 1, 2008.
- 

**Complex Behavior of Switching Power Converters,**  
 Chi Kong Tse, CRC Press, 2004.

24/25

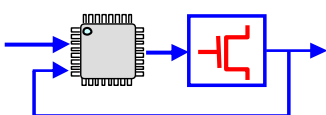

808-PowerLab NCTU HSINCHU TAIWAN

## References: Modeling of DC-DC Converters

**Recommended Readings**

- [1] D. Maksimovic, A. M. Stankovic, V. J. Thottuvelil, G. C. Verghese, "Modeling and simulation of power electronic converters," *Proceedings of the IEEE*, vol. 89, no. 6, pp. 898-912, June 2001.
- [2] A. J. Forsyth and S. V. Mollov, "Modelling and control of DC-DC converters," *IEEE Power Engineering Journal*, vol. 12, no. 5, pp. 229-236, 1998.
- [3] R. D. Middlebrook, "Small-signal modeling of PWM switched-mode power converters," *IEEE Proc.* vol. 76, no. 4, pp. 343-354, April 1988.
- [4] R. D. Middlebrook and S. C'uk, "A general unified approach to modeling switching converter power stages," *IEEE PESC Conf. Rec.*, pp. 18-34, 1976. [Pioneer paper]

**SPS Modeling and Control Loop Design**

- [5] V. Vorperian, "Simplified Analysis of PWM Converters Using Model of PWM Switch Part I: Continuous Conduction Mode," *IEEE Trans. on Aero. and Electron. Sys.*, vol. 26, no. 3, pp. 490-496, May 1990.
- [6] V. Vorperian, "Simplified Analysis of PWM Converters Using Model of PWM Switch Part II: Discontinuous Conduction Mode," *IEEE Trans. on Aero. and Electron. Sys.*, vol. 26, no. 3, pp. 497-505, May 1990.
- [7] V. Voperian, R. Tymerski, and F. C. Lee, "Equivalent circuit models for resonant and PWM switches," *IEEE Trans. on Power Electronics*, vol. 4, no. 2, pp. 205-214, April 1989.
- [8] E. Van Dijk, J. N. Spruijt, D. M. O'Sullivan, and J. B. Klaassens, "PWM-switch modeling of DC-DC converters," *IEEE Transactions on Power Electronics*, vol. 10, no. 6, pp. 659-665, Nov 1995.

**Modeling of Switching Converters in DCM Operation**

- [11] D. Maksimovic and S. Cuk, "A unified analysis of PWM converters in discontinuous modes," *IEEE Trans. Power Electron.*, vol. 6, pp. 476-490, May 1991.
- [12] J. Sun, D. M. Mitchell, M. F. Greuel, P. T. Krein, and R. M. Bass, "Averaged modeling of PWM converters operating in discontinuous conduction mode," *IEEE Trans. Power Electron.*, vol. 16, pp. 482-492, July 2001.

25/25

808-PowerLab NCTU HSINCHU TAIWAN



**808-PowerLab. NCTU**  
 Power Electronic Systems & Chips Lab., NCTU, Taiwan



## Any Questions ???

Questions inspire effective learning!



學習的關鍵

- 記筆記
- 問問題



電力電子系統與晶片實驗室

Power Electronic Systems & Chips Lab.

交通大學 • 電機與控制工程研究所

26/25

